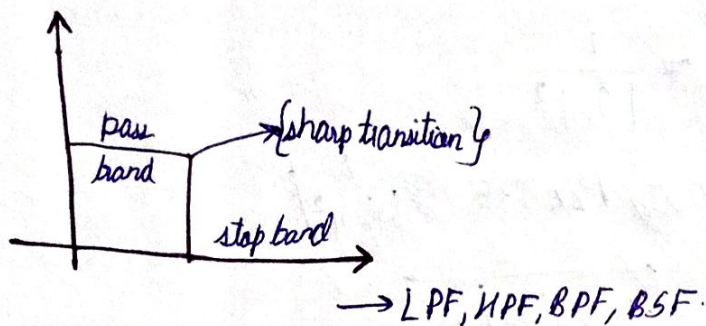



Microwave filter



In practical filter;

Gradual transition, from:-


Passband to stopband or vice versa.

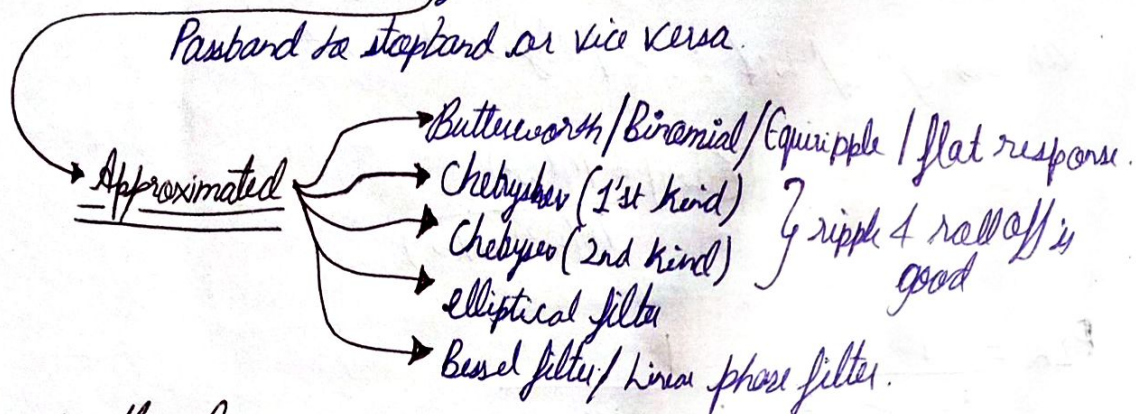

Insertion loss method :-

(to design Microwave filter)
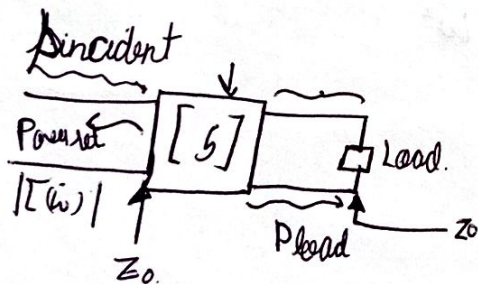
$$\text{Power loss ratio (PLR)} = \frac{\text{Power available from the source}}{\text{Power delivered to the load}}$$



$$PLR = \frac{P_{inc}}{P_{inc} - P_{ret}} = \frac{1}{1 - \frac{P_{ret}}{P_{inc}}} = \frac{1}{1 - |\Gamma(w)|^2}$$

$$|\Gamma(w)|^2 = \left| \frac{\gamma_{ret}}{\gamma_{inc}} \right|^2$$

$$|S_{11}|^2 + |S_{21}|^2 = 1 \rightarrow \text{lossless}$$

$$|S_{21}|^2 = 1 - |S_{11}|^2$$

For matched condⁿ at both ports, $|T(\omega)|$ can be written as $|S_{11}|$

$$P_{LR} = \frac{1}{1 - |S_{11}|^2} = \frac{1}{|S_{21}|^2}$$

$$\text{Insertion loss (IL)} = 10 \log P_{LR} = 10 \log \frac{1}{|S_{21}|^2}$$

$$= \boxed{-20 \log |S_{11}|}$$

It can be shown that $|T(\omega)|^2$ is an even fⁿ of ω . So $|T(\omega)|^2$ can also be a polynomial in ω^2 .

$$|T(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}$$

$$P_{LR} = \frac{1}{1 - |T(\omega)|^2} = \frac{1}{1 - \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}}$$

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

where M & N are real polynomial in ω^2 .

Maximally flat / Butterworth filter.

$$P_{LR} = 1 + k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

$k \rightarrow$ ripple factor


$\omega \rightarrow$ any angular freq.

$\omega_c \rightarrow$ angular cutoff freq.

$N \rightarrow$ order of filter.

if $k=1$ & $\omega = \omega_c$

$$P_{LR} = 1 + (1)^{2N} = 2$$

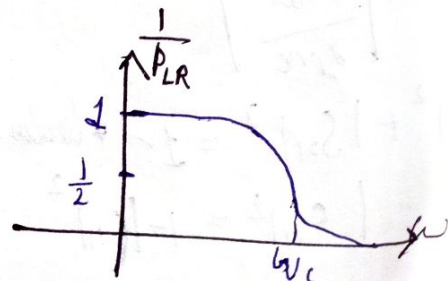


For large ω & $k=1$,

$$P_{LR} = 1 + \left(\frac{\omega}{\omega_c}\right)^{2N} = \left(\frac{\omega}{\omega_c}\right)^{2N}$$

$$IL = -20 \log |S_{21}| = -20 \log \frac{1}{\sqrt{P_{LR}}} = 10 \log P_{LR}$$
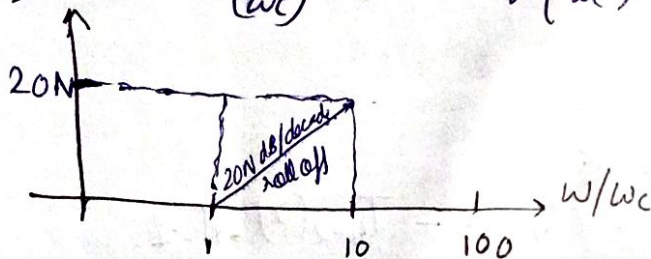
$$= 10 \log \left(\frac{\omega}{\omega_c}\right)^{2N} = 20N \log \left(\frac{\omega}{\omega_c}\right)$$



Microwave filter:-

Insertion loss: $IL (dB) = 10 \log P_{LR}$

@ Butterworth filter, $P_{LR} = 1 + K^2 \left(\frac{\omega}{\omega_c}\right)^{2N}$

$\omega > \omega_c$; $P_{LR} \approx K^2 \left(\frac{\omega}{\omega_c}\right)^{2N}$

for $K^2 = 1$, {Ripple factor}

$$P_{LR} = \left(\frac{\omega}{\omega_c}\right)^{2N}$$

$$\Rightarrow IL = 10 \log \left(\frac{\omega}{\omega_c}\right)^{2N}$$

$$\frac{IL}{10} = 2N \log \left(\frac{\omega}{\omega_c}\right)$$

now, given $f_c = 400 \text{ MHz}$

@ $f = 1 \text{ GHz}$

$IL = 20 \text{ dB}$

$$N = \frac{\log(10^{IL/10})}{2 \log \left(\frac{\omega}{\omega_c}\right)}$$

Chebyshev filter

$$P_{LR} = 1 + k^2 T_N^2\left(\frac{\omega}{\omega_c}\right)$$

$T_N(x) \rightarrow$ Poly factor: is a Chebyshev poly 1st kind
2nd kind

oscillatory f^n for $x \in [-1, 1]$ beyond which, it increases monotonically.

1st Kind Chebyshev Polynomial:

$$T_0(x) = 1$$

$$T_1(x) = x$$

$$T_N(x) = 2x(T_{N-1}(x) - T_{N-2}(x)), N > 1$$

@ $N=2$,

$$T_2(x) = 2x^2 - 1$$

$$T_3(x) = 2x(2x^2 - 1) - x = 4x^3 - 3x$$

$$T_4(x) = 2x(4x^3 - 3x) - (2x^2 - 1) = 8x^4 - 8x^2 + 1$$

and so on.

diff. between the first & second kind only exists for $T_1(x)$ that is,
 $T_1(x) = 2x$ for second kind.

@ $-1 < x < 1$


$$T_0(x) = 1$$

$$T_1(x) = [-1, 1]$$


$$T_2(x) = [-1, 1]$$

$$T_3(x) = [-1, 1]$$

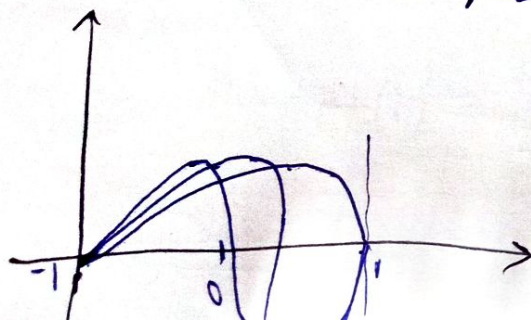we will always get $[-1, 1] \rightarrow$ oscillating values.
 Chebyshev can also be represented trigonometrically.




Can be something like this.

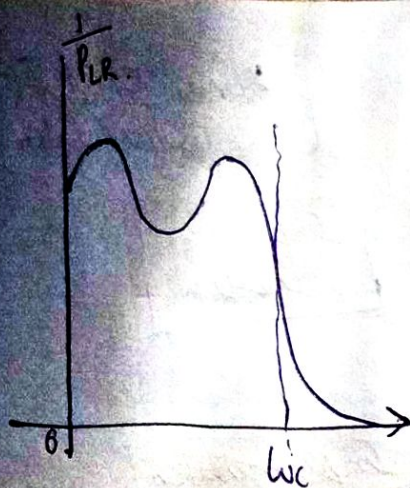

← we did not consider the -ve frequency. we are concerned only about the +ve ones.

order	P_{LR}
$2nd/N=2$	$1 + k^2 T_2^2(w/w_c)$ $= 1 + k^2 \left(2 \left(\frac{w}{w_c} \right)^2 - 1 \right)^2$ @ $w=0, P_{LR} = 1 + k^2$ @ $w = w_c, P_{LR} = 1 + k^2$
$N=3$	$1 + k^2 \left(4 \left(\frac{w}{w_c} \right)^3 - 3 \left(\frac{w}{w_c} \right) \right)^2$

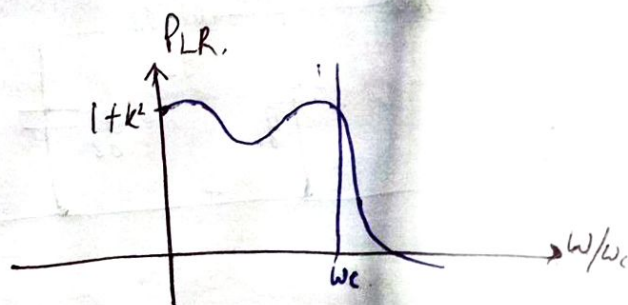

→ @ even order filter,
 $w=0$ & $w=w_c$
 $\Rightarrow P_{LR} = 1 + k^2$ @
 odd filter
 $w=0 \Rightarrow P_{LR} = 1$

for w is large

$$P_{LR} = \frac{k^2}{4} \left(\frac{2w}{w_c} \right)^{2N} \rightarrow \text{Chebyshev.}$$


@ Butterworth, $P_{LR} \approx k^2 \left(\frac{w}{w_c} \right)^{2N}$ @ w is large.

P_{LR} is more in Chebyshev by a factor of $2^{2N}/4 \rightarrow$ IL in Chebyshev = $10 \log \frac{2^{2N}}{4}$ dB



$$N = \frac{\log 10^{IL/10} \times 4/k^2}{2 \log(w/w_c)}$$

more than BW.

General procedure to design a filter:

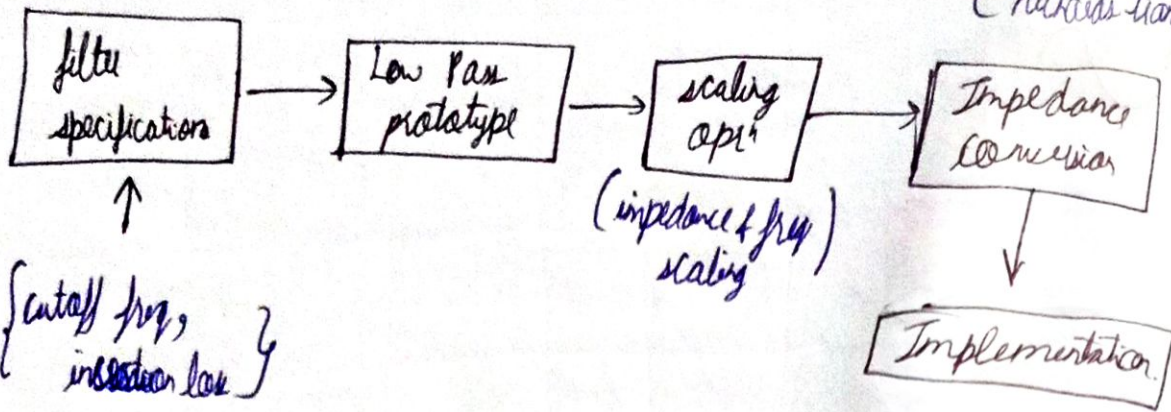

Realizing LPF prototype

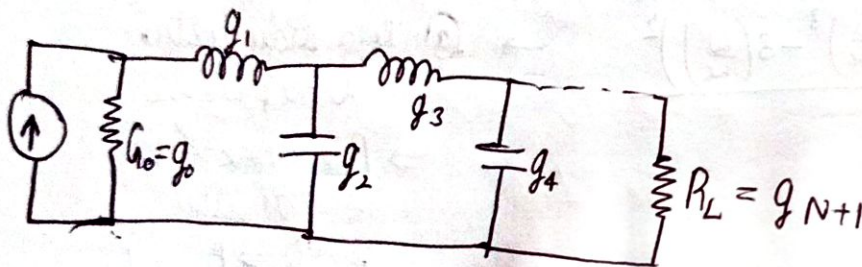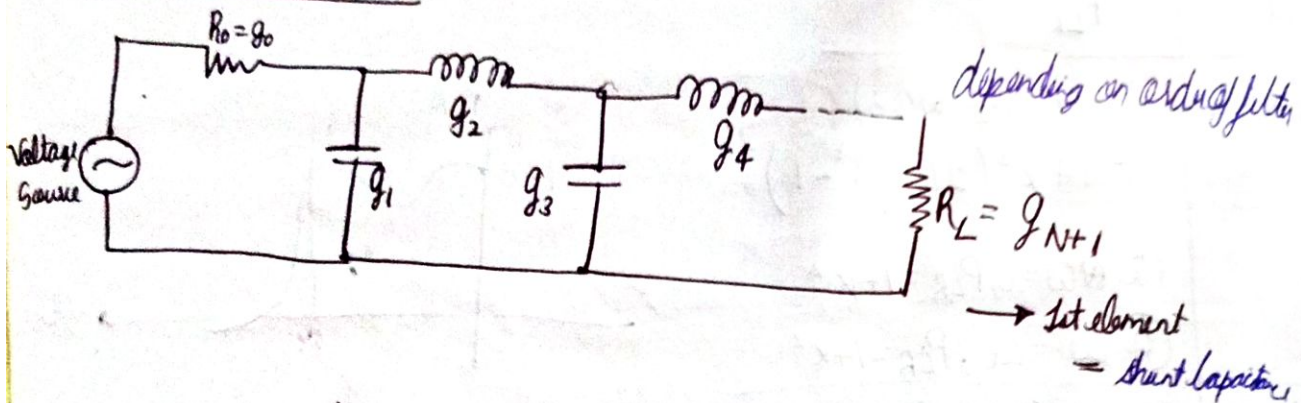

g → generator, g_0 → source impedance
 N → order of the filter g_{N+1} → load imp.
 we get g_1, g_2, g_3 and so on.

$$R_L' = 1 \cdot R_0 = R_0$$

$$R_L' = 1 \cdot R_0 = R_0$$

or sometimes (when $R_L \neq 1$)

$$R_L \cdot R_0 = R_L \cdot R_0$$

② Frequency scaling:-

Here we replace ω by $\frac{\omega}{\omega_c}$

$$X_L = \omega L$$

$$X_L' = \frac{\omega L}{\omega_c} = \omega L'$$

$$\therefore L' = \frac{L}{\omega_c}$$

$$L' = \frac{g_k}{\omega_c}$$

$$X_C = \frac{1}{\omega C}$$

$$X_C' = \frac{\omega_c}{\omega \cdot C} = \frac{1}{\omega C'}$$

$$\therefore C' = \frac{C}{\omega_c}$$

$$C' = \frac{g_k}{\omega_c}$$

same

Applying Impedance + freq. scaling both:

$$\begin{aligned} L_k' &= \frac{L_k R_o}{\omega_c} \\ C_k' &= \frac{C_k}{R_o \omega_c} \end{aligned}$$

Finding g -parameter for Butterworth LPF prototype:-

$$g_0 = g_{N+1} = 1 \text{ (normalized value)}$$

$$g_k = 2 \sin \left[\frac{(2k-1)\pi}{2N} \right], k = 1, 2, 3, \dots, N$$

T_N

$\frac{1}{\omega}$

	g_0	g_1	g_2	g_3	g_4	g_5
$N=1$	1	2	1			
$N=2$	1	1.414	1.414	1		
$N=3$	1	1	2	1	1	
$N=4$	1	0.7658	1.847	1.847	0.7654	1

Impedance scaling

Voltage
Gauss

→ multiply impedance by R_0 (Characteristic resistance)

$$X_L = \omega L$$

Applying impedance scaling

$$X_L' = \omega L R_0 = \omega L'$$

$$\therefore L' = L R_0 \text{ (new inductance after impedance scaling)} \\ = g_k R_0$$


$$X_C = \frac{1}{\omega C}$$

$$X_C' = \frac{1}{\omega C} \times R_0$$

↓

$$\frac{1}{\omega C'} = \frac{1}{\omega \left(\frac{C}{R_0} \right)}$$
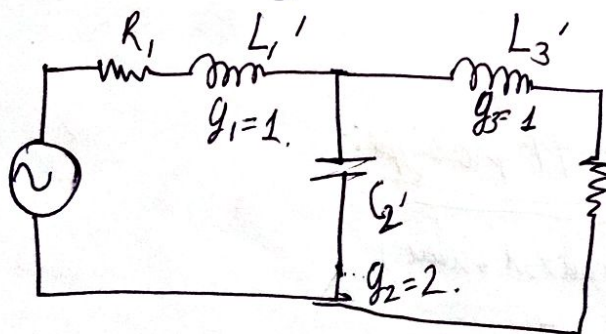
$$\therefore \boxed{C' = \frac{C}{R_0}} \quad C' = \frac{g_k}{R_0}$$



$$\text{Given: } R_0 = 50 \Omega$$

$$f_c = 36 \text{ kHz}$$

g parameters
(N=3)

$$L_k' = \frac{L_k R_o}{\omega_c}$$


$$C_k' = \frac{C_k}{R_o \omega_c}$$

$$L_1' = (g_1 + 50) / 2\pi \times 3 \times 10^9 = 2.653 \times 10^{-9} \text{ H}$$

$$C_2' = (g_2 \times 1) / 50 \times 2\pi \times 3 \times 10^9 = 2.123 \times 10^{-12} \text{ F}$$

$$L_3' = (g_3 \times 50) / 2\pi \times 3 \times 10^9 = 2.653 \times 10^{-9} \text{ H}$$

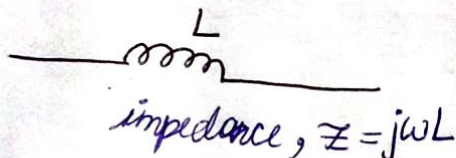
Filter Implementation [Richard's Transformation]



$$Z_{in} = Z_o \left[\frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \right]$$

$$\text{If } l = \frac{\lambda_c}{8}$$

Considering,

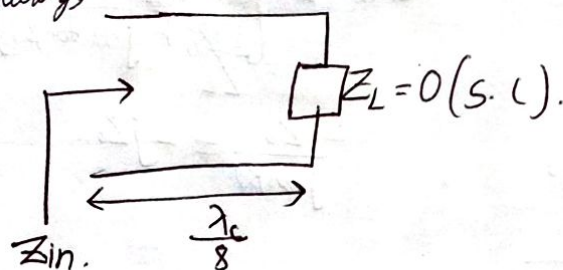

equating the impedances,


$$jZ_o = j\omega_c L$$

$$\boxed{Z_o = \omega_c L} \text{ (to get the characteristic impedance)}$$

$$Z_L = 0, Z_{in} = jZ_o \tan \beta l$$

$$Z_{in} = jZ_o \text{ (purely inductive)}$$

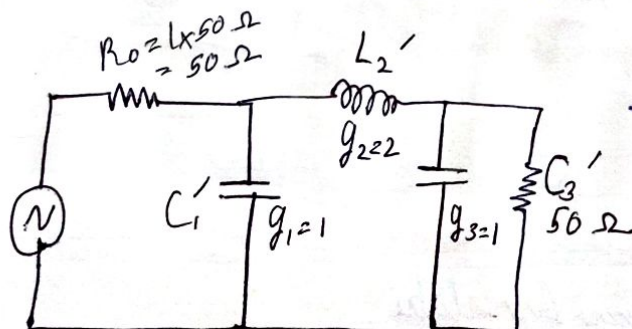Design a maximally flat filter $\rightarrow$ another name of Butterworth.
 $f_c = 400 \text{ MHz}$





$IL @ 1 \text{ kHz} = 20 \text{ dB}$, $R_o = R_L = 50 \Omega$
(we found in last class
order of filter = 3)

$$C_1' = \frac{g_1}{R_o \omega_c} = \frac{1}{50 \times 2\pi \times 400 \times 10^6} = 7.96 \text{ pF}$$

$$L_2' = \frac{g_0 R_0}{\omega_c} = \frac{1}{8\pi \times 10^6} = 39.8 \text{ nH}$$
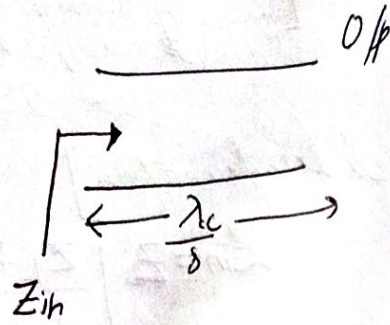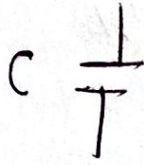
$$C_3 = \frac{g_3}{R_0 \omega_c} = 7.95 \text{ pF}$$



$$Z = \frac{1}{j\omega_c C} = -\frac{j}{\omega_c C}$$

$$Z_L = \infty$$

$$Z_{in} = Z_0 \left[\frac{1 + j \frac{Z_L}{Z_0} \tan \beta l}{\frac{Z_0}{Z_L} + j \tan \beta l} \right]$$


$$= \frac{Z_0}{j \tan \beta l} = -j Z_0$$

equating,

$$\frac{-j}{\omega_c C} = -j Z_0$$

$$\therefore \boxed{Z_0 = \frac{1}{\omega_c C}}$$

Realizing the prev. network

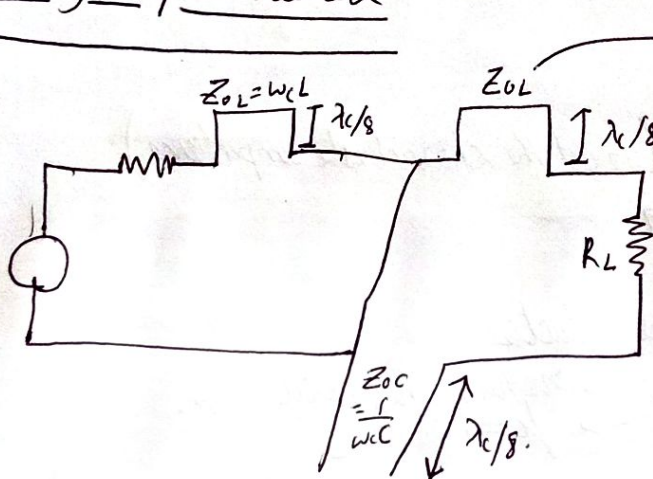


for chebyshev we would have had diff. g parameters and hence diff. values Z_{0L} for diff. inductors

Kuroda Identity


Advantages:

- It physically separate transmission line stubs.
- Transform series stub to shunt stub & vice versa.
- Change impractical characteristic impedance into more realizable impedance.


1st Kuroda Identity:

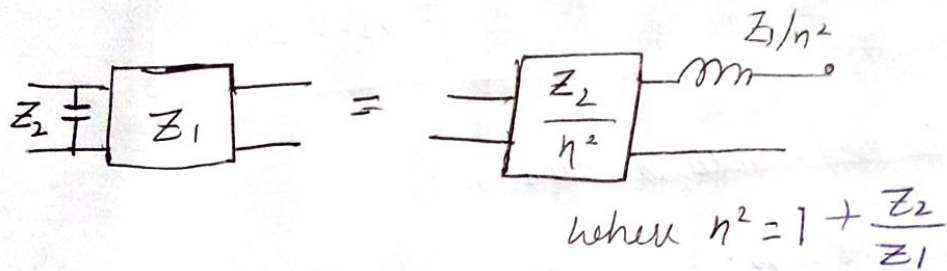

2nd Kuroda Identity:

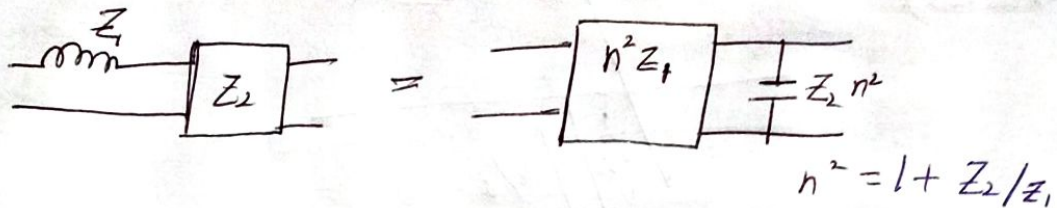

in the prev. n/w, we have

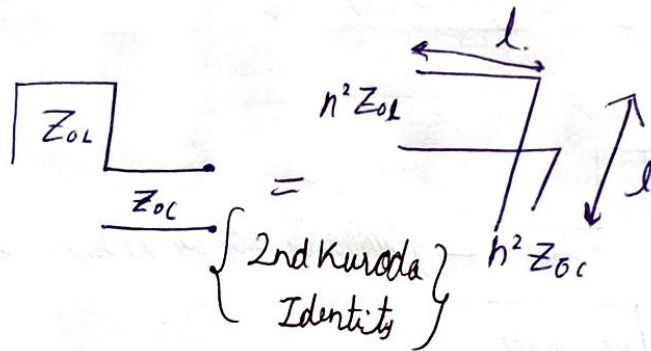

Chebyshev / Equal ripple filter

N	g_1	g_2	g_3
1	-	-	-
2	-	-	-
3	3.3487	0.7117	3.3487

Problem 1 → Design a 3dB ripple low pass filter using microstrip line - - -
Specifications are:


Cutoff freq. = 4 GHz

Order of the filter = 3

Characteristic impedance

@ source load = 50 Ω
(R_s & R_L)


step 1: - Find g parameters for

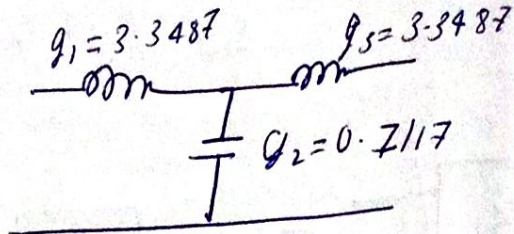


(we are using normalized value in)

step 2: - Realize the n/w:


$W_L = 1$ (normalized)

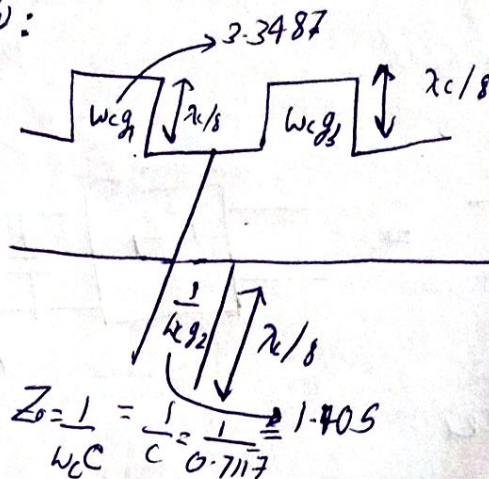

step 3:

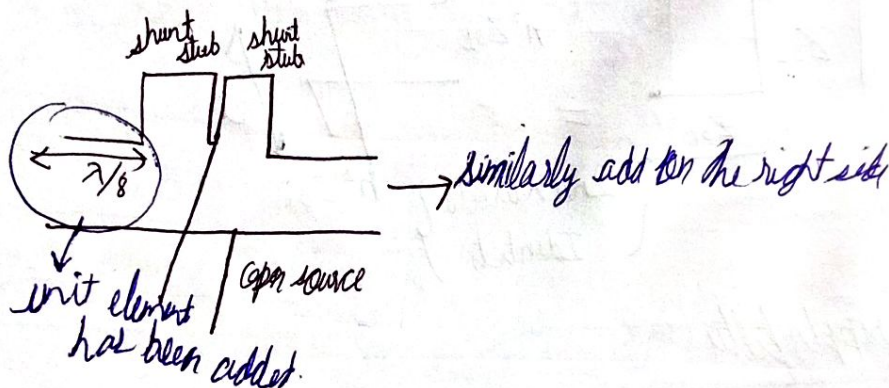

step 4: Apply 2nd Kuroda identity


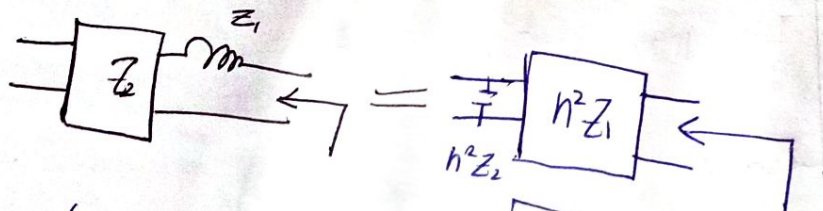


(trans) $n^2 Z_1 = (1.298)(3.3487) = 4.35$
 (Cap) $n^2 Z_2 = (1.298)(1) = 1.298$

$n^2 = 1 + \frac{Z_2}{Z_1}$

similarly for second stub.
 trans $\rightarrow 4.35$ and
 Cap $\rightarrow 1.298$

$n^2 = 1 + \frac{1}{3.3487} = 1.298$

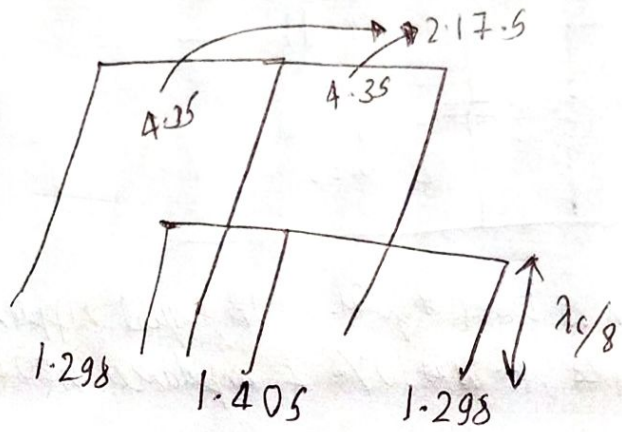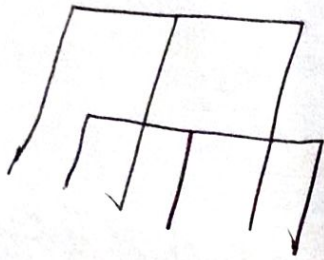

$$\lambda_c = \frac{c}{f} = \frac{3 \times 10^8}{4 \times 10^9}$$


$$= 7.5 \text{ cm}$$

$\Downarrow$
 multiplying the imp. to find
 correct value, $L_1 = 1.298 \times 50$
 $= L_3 = 64.9 \Omega$
 $C_2 = 1.405 \times 50$
 $= 70.3 \Omega$


Input $\rightarrow$ S.T.L

Transformation from LPF to HPF, BPF, BSF


LPF

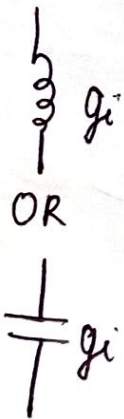


HPF

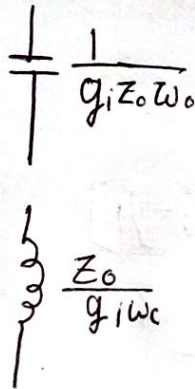



BPF

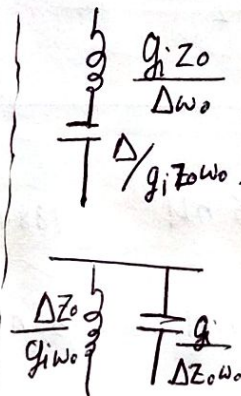

BSF

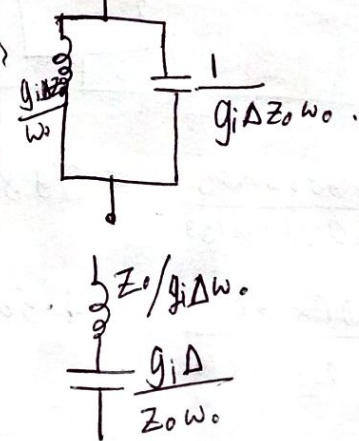



eg - 3rd order:

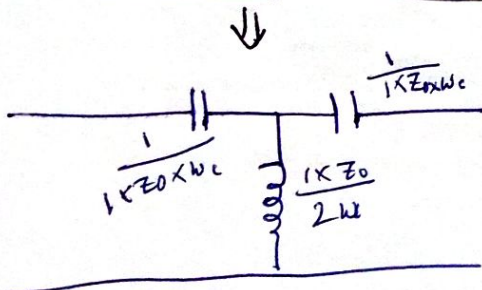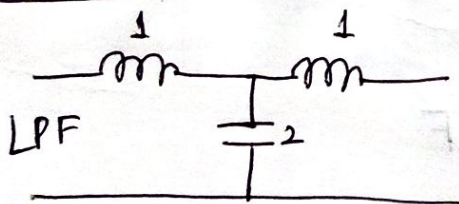

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$$



$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

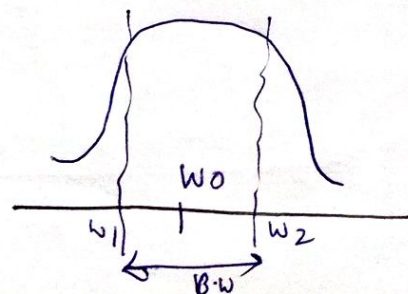

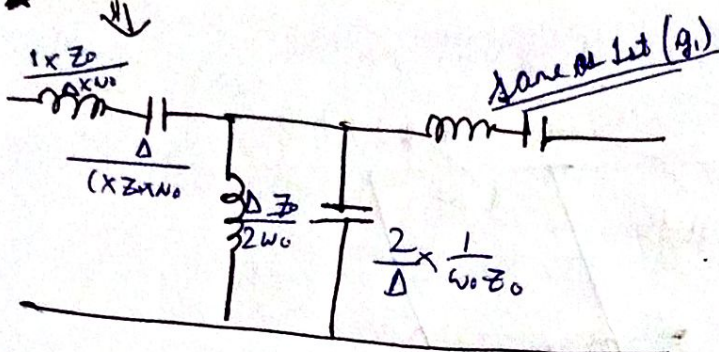

Q - Design a bandpass filter. 0.5 dB equal ripple response with order of 3. The center frequency is 1 GHz, B.W is 10% & impedance is 50 Ω .

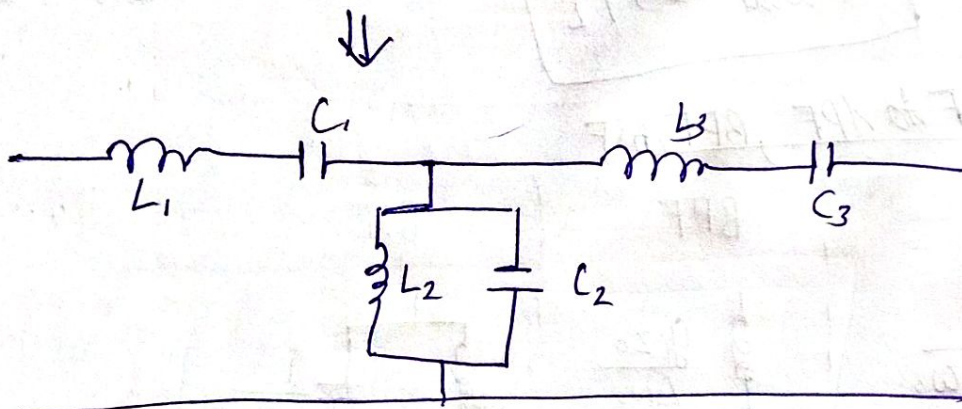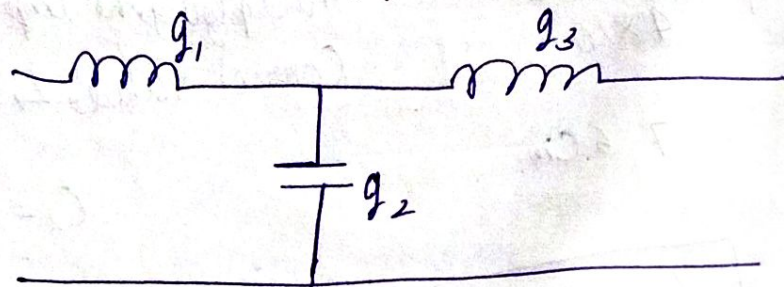Given, $g_1 = 1.5963$, $g_2 = 1.0967$, $g_3 = 1.5963$



$$L_1 = \frac{1.5963 \times 50}{(0.1) \times 1 \times 10^9} = 798.15 \text{ nH} \quad [798.15 \times 10^{-9} \text{ H}]$$

$$L_2 = \frac{(0.1) \times 50}{1.0967 \times 1 \times 10^9} = 4.569 \text{ nH} \approx 4.56 \text{ nH} \quad [4.56 \times 10^{-9} \text{ H}]$$

$$C_1 = \frac{(0.1)}{1.5963 \times 50 \times 1 \times 10^9} = 12.52 \text{ pF} \quad [0.00125 \times 10^{-9} \text{ F}]$$

$$C_2 = \frac{1.0967}{(0.1)(50)(10^9)} = 0.2193 \text{ nF} = 219.3 \text{ pF}$$